
NSSA-102 Computer system Concepts

Qusai Hasan

Midterm Worksheet

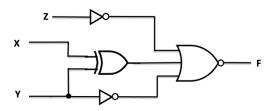- 1) If N = 8A.2B in hexadecimal, what is N in octal?
- 2) If N = 123.11 in base r=4, what is the value of N in decimal?
- 3) If N = 34.02 in decimal, what is N in base r=5? ______
- 4) If N = 606 in decimal, what is N in BCD? _____
- 5) What is the minimal number of bits needed to assign binary codes to 71 colors?
- 6) Draw the logic circuit for the Function $F(A, B, C) = \bar{A} + \bar{B} (A \oplus C)$
- 7) Fill-in the truth table for the Function $F(A, B, C) = \bar{A} + \bar{B} (A \oplus C)$
- 8) Write down the equation of the below logic circuit as a sum-of-minterms (SoM)?



9) Using Boolean algebra, prove that

$$\overline{x} + xy + x\overline{z} + x\overline{y}\overline{z} = \overline{x} + y + \overline{z}$$

10) Using Boolean algebra, determine the product-of-maxterms (PoM) expression for


$$F(A,B,C) = (A+B) (\bar{C} + \bar{A}B)$$

11) Let $F(A, B, C) = M_3 . M_5 . M_7$

Write $\bar{F}(A, B, C)$ as a SoM expression.

12) Given
$$F(A, B, C) = (A + B)(\bar{C} + \bar{A}B)$$
. Determine $\bar{F}(A, B, C) = \sum_{m} ($

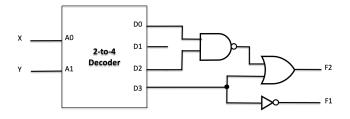- 13) Fill-in the truth table for the function $F(A, B, C) = \overline{A + \overline{B} C}$
- 14) Fill-in the truth table for the function $F(A,B,C)=\bar{A}\odot(B+A\bar{C})$
- 15) Fill-in the truth for the below circuit.



Х	Υ	F1	F2
0	0		
0	1		
1	0		
1	1		

16) Write the equation of F(A,B,C) as a sum-of-minterms for the below circuit.

